

**Name and Student ID: Rafat Momin 593070532**

**Lab Section: 7**

**Date: 12/7/23**

**Net ID: rafatmom**

**Submission Instructions:**

**Prelab:**

- 1. No prelab**


**Lab:**

- 1. Complete the scavenger hunt according to the instructions**
- 2. Take screenshots of each component and include them in the document below (note: to receive points your NetID has to be visible in the screenshot, say in a command window that is in the background).**
- 3. Complete this document and upload it to Canvas**

### Part 1: CPU Scavenger Hunt

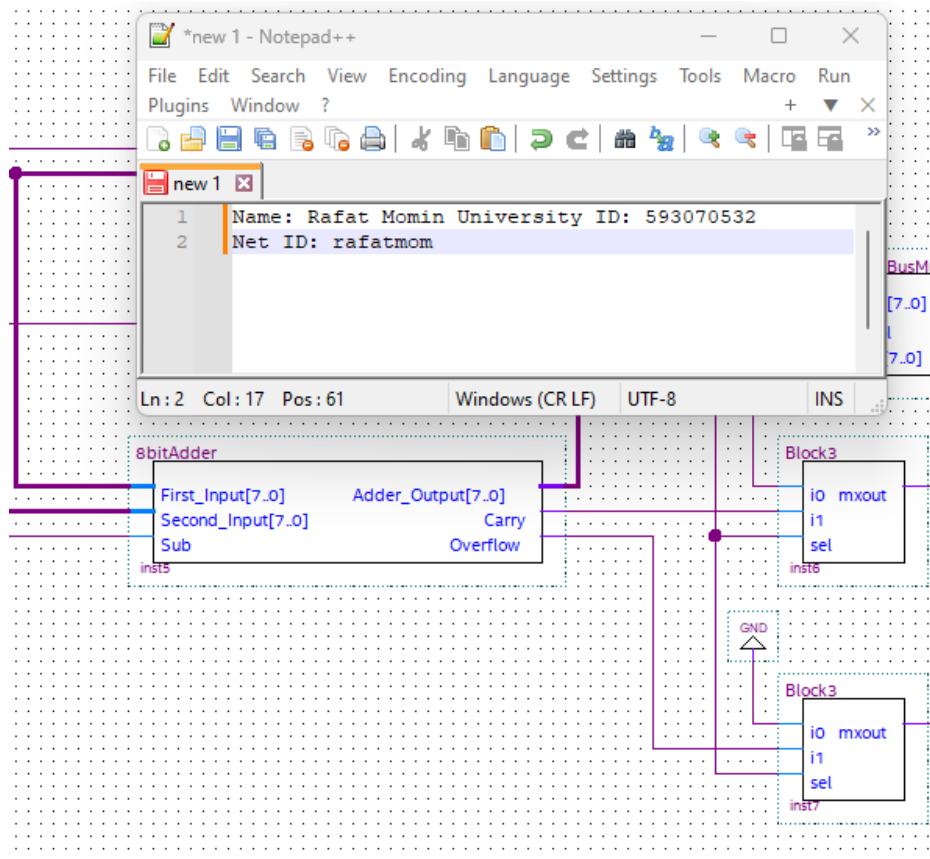**Q1.** Find the **adder** inside the ALU and answer the following:

- What is the name of this component?
- **Answer:** 8-bit adder
- Is it a ripple-carry or carry lookahead adder?
- **Answer:** Ripple-carry
- Can it also do subtraction?
- **Answer:** Yes, it can. (Because of XOR)
- What is the size of its two operands in bits?
- **Answer:** 8 bits
- <<< screenshot of the adder symbol >>>




- **Screenshot for Q1**

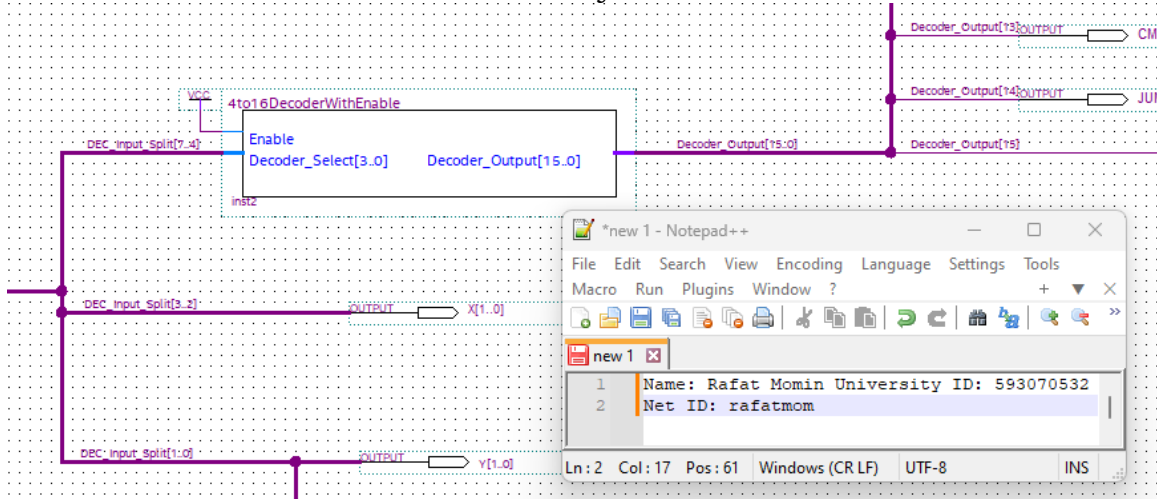**Q2.** Find a 4-to-16 **decoder** and answer the following:

- What is the name of this component?
- **Answer:** 4to16DecoderWithEnable
- Does it have an enable input?  
**Answer:** Yes
- What are the names of its outputs 4 and 6?
- **Answer:** 4 is Add, and 6 is Sub.
- Can you guess what is its function in this CPU?
- **Answer:** It helps to decide whether an addition or a subtraction will happen based on the output of the instruction memory.


- <<< screenshot of the decoder symbol >>>



**Screenshot for Q2**

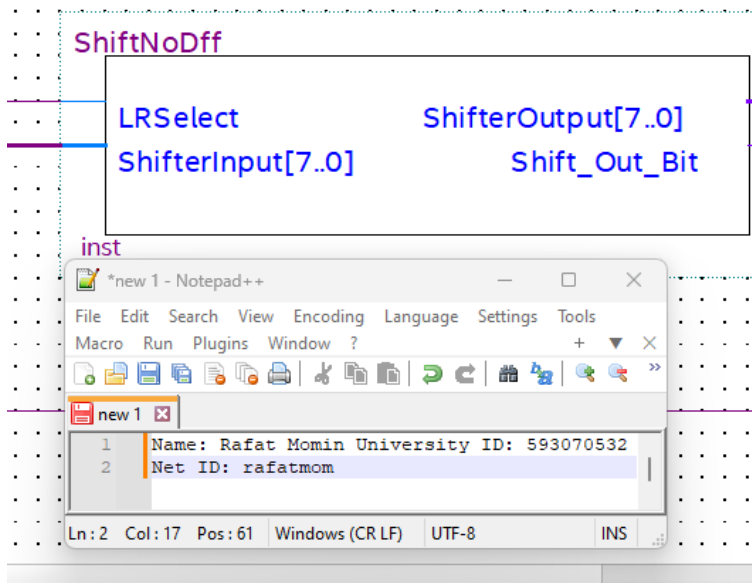**Q3.** Find a **shifter circuit** and answer the following:


- What is the name of this component?  
• **Answer:** ShiftNoDFF
- What is the size of the input in bits?  
• **Answer:** 8
- What happens to the most significant bit on shift left?  
**Answer:** It takes the most significant bit out of the circuit to the output.
- What happens to the least significant bit on shift right?  
• **Answer:** It takes the least significant bit out the circuit to the output.
- <<< screenshot of the shifter symbol >>>



- **Screenshot for Q3**

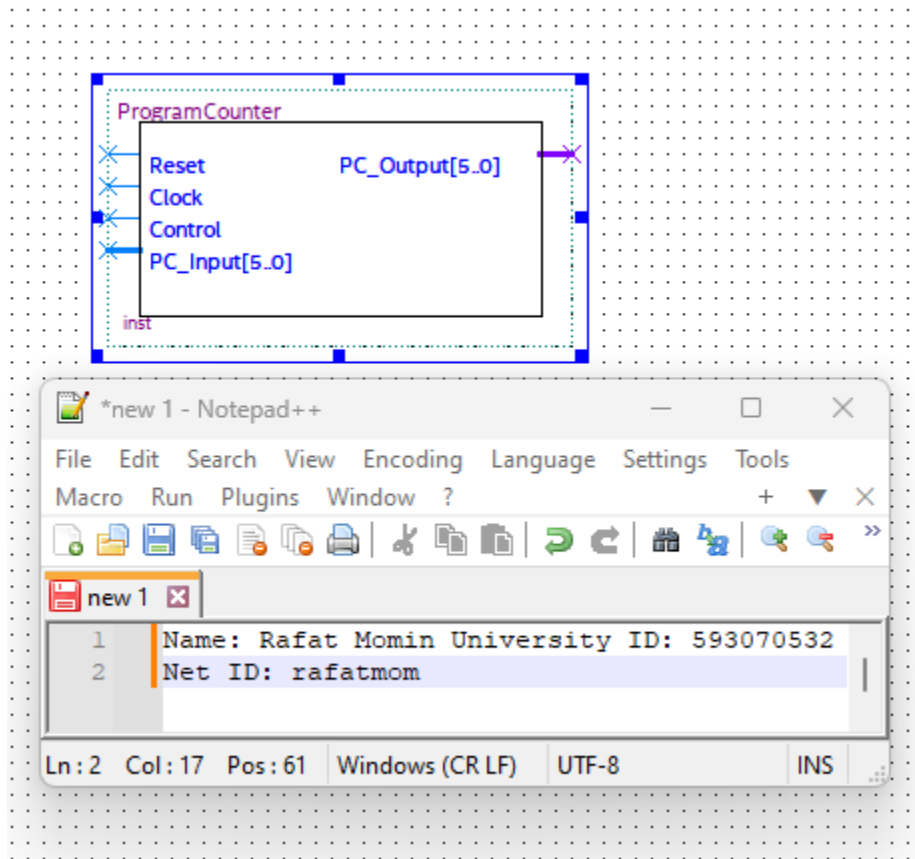**Q4.** Find the **program counter** and answer the following:

- What is the name of this component?
- **Answer:** ProgramCounter
- What is the size of the output bus in bits?
- **Answer:** 6
- How many control lines does it have?
- **Answer:** 1
- What type of high-level circuit does it implement?
- **Answer:** Parallel Load Resgister
- <<< screenshot of the program counter symbol >>>




**Screenshot for Q4**

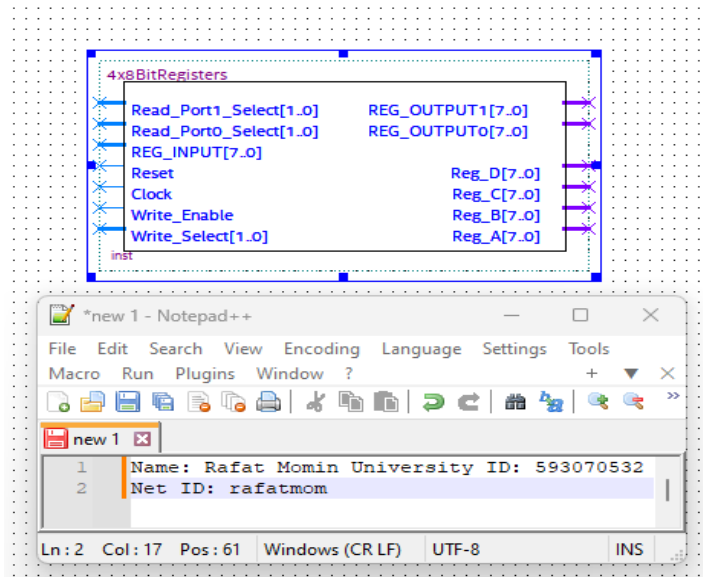**Q5.** Find a **register file** with exactly 4 registers and answer the following:

- What is the name of this component?
- **Answer:** 4x8BitRegisters
- What is the size of each register in bits?
- **Answer:** 8 bits
- What type of Flip-Flops are used to construct each register?
- **Answer:** D flip-flop
- The contents of how many registers can be read at the same time?
- **Answer:** 2


- <<< screenshot of the register file symbol >>>



- **Screenshot for Q5**

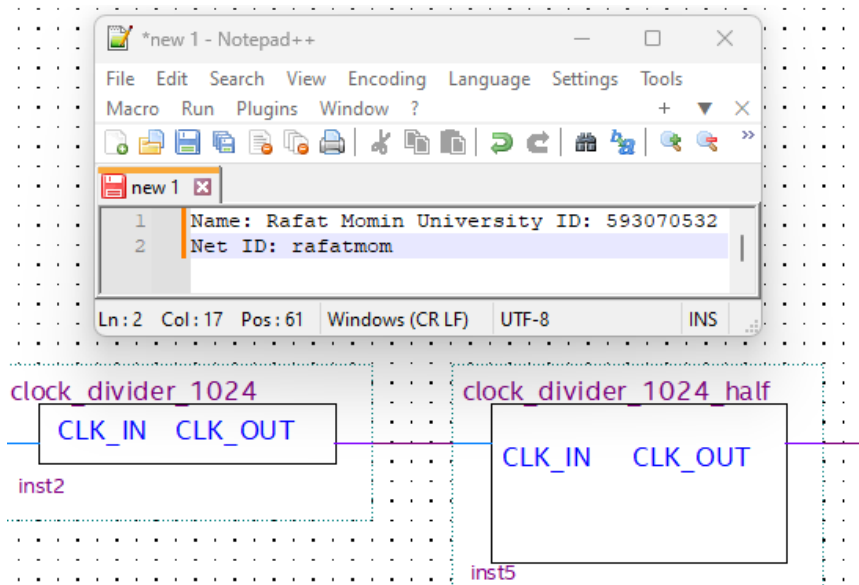**Q6.** Find the two **clock dividers** for the **VideoGame\_Clock** and answer the following:

- How are they implemented?
- **Answer:** It has 10 flip-flops and the clock-divider is a counter, implemented with counters.
- They slow down the clock by a factor of X and Y. What are X and Y?
- **Answer:** X= 512, Y= 1024. The reason is : every total clock cycle takes about  $2^9$  for the counter to go through the cycle of the 8 bit combinations. Therefore, X = 512 (the first bit remains intact). And for the second factor, it could also reset the whole cycle of the 9 bits so it is  $2^{10} = 1024$ .
- <<< screenshot of the two clock dividers >>>




Screenshot for Q6

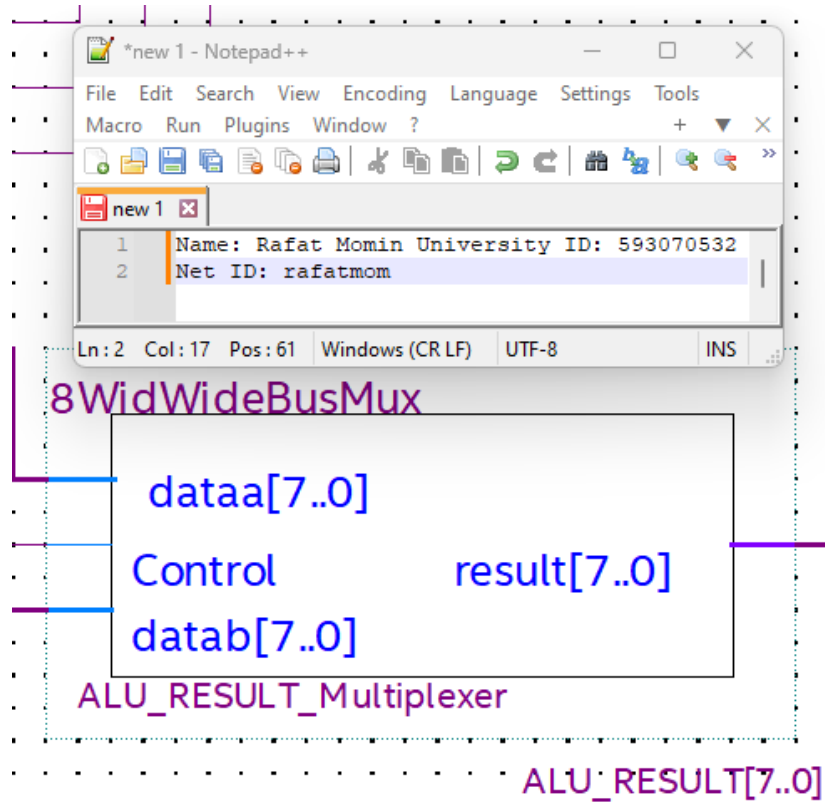**Q7.** Find the **multiplexer** that sits after the ALU and takes the output of the ALU as one of its inputs. Then, answer the following:

- What is the name of this component?
- **Answer:** 8WidWidebusMux
- Where does the other input come from?
- **Answer:** From the box IMEM. (It is taking 8 bits out of the 16).
- What is the size of each input in bits?
- **Answer:** 8
- How many select lines does it have in bits?
- **Answer:** A single line.
- <<< screenshot of the multiplexer symbol >>>






- **Screenshot for Q7**

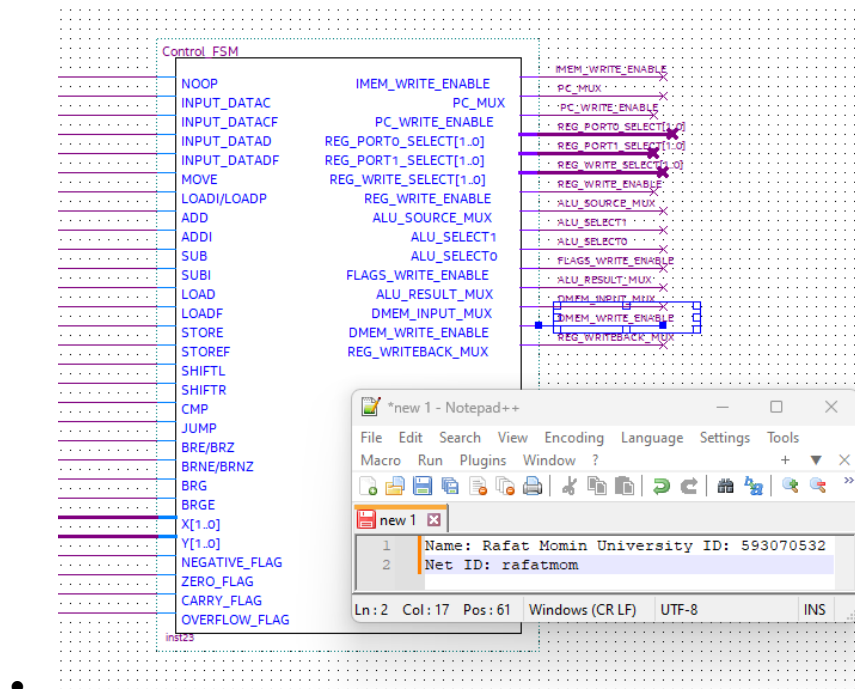**Q8.** Find the circuit that outputs the signal **DMEM\_WRITE\_ENABLE** and then answer the following:


- In which block is this circuit located?
- **Answer:** Control FSM.
- What is the Boolean expression for this signal?  
**Answer:**  $\text{INPUT\_DATAD} + \text{INPUT\_DATAF} + \text{STOREF} + \text{STORE}$
- <<< screenshot of the block in which the circuit is located >>>



• **Screenshot for Q8**

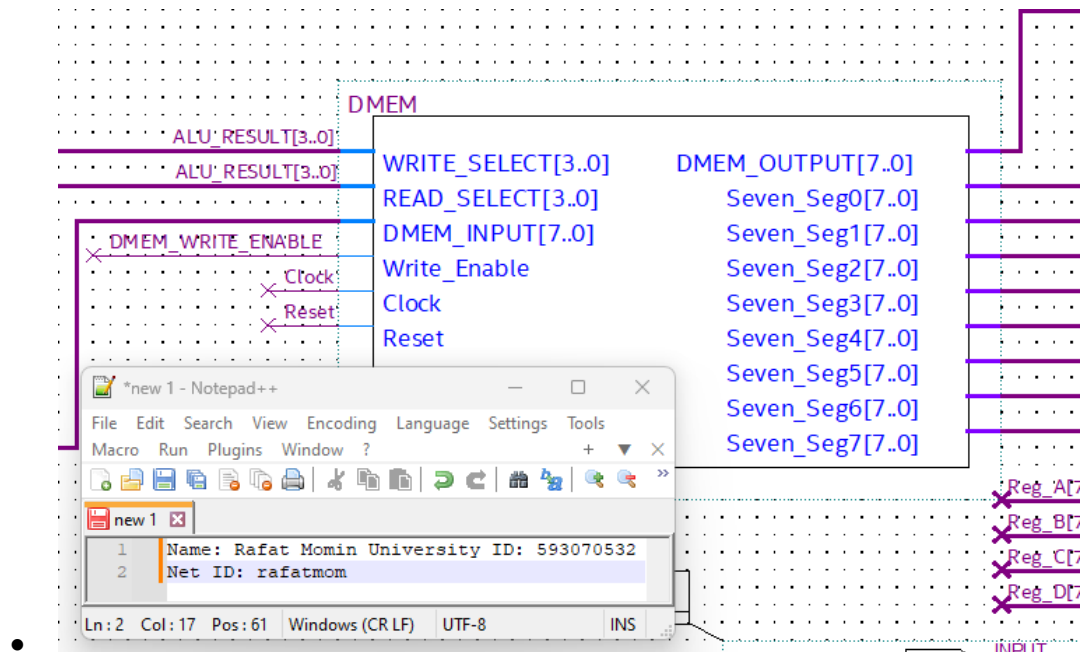**Q9.** Examine the **DMEM** box and answer the following:

- What are the names of the control lines for this box?
- **Answer:** READ\_SELECT[3..0]
- WRITE\_SELECT[3..0]
- What the high-level component is used to store the data?
- **Answer:** Register file
- What is the size of the data memory in bytes?
- **Answer:** 16 bytes
- <<< screenshot of the high-level component symbol >>>



• **Screenshot for Q9**

**Q10.** Find the **flags register** and answer the following:


- How many flags does it store?

**Answer:** 4

- What are the names of these flags?

**Answer:** Negative\_Flag, Zero\_Flag, Carry\_Flag, Overflow\_flag

- <<< screenshot >>>

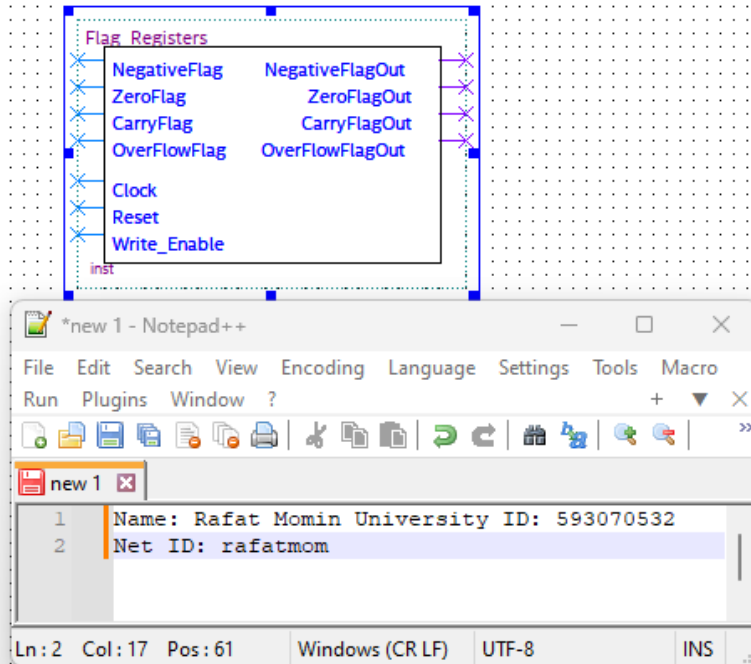

**Screenshot for Q10**

**Part 2: PONG.** Take a cellphone picture of the board as you are playing the game. Selfies are OK too as long as the game is visible in the background ☺

- <<< picture >>>



**Screenshot for Part 2**